# Control Systems

G V V Sharma\*

1


#### **CONTENTS**

#### 1 Feedback Circuits

Abstract—The objective of this manual is to introduce control system design at an elementary level.

# 1 FEEDBACK CIRCUITS

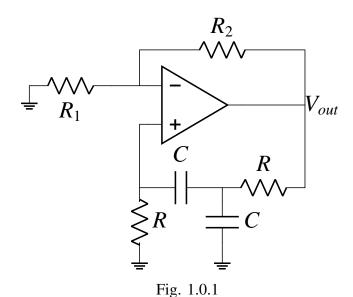1.0.1. For the Wein-bridge oscillator of Fig 1.0.1, use the expression for loop gain in Eq 1.0.3.5 to find the poles of the closed-loop system. Give the expression for the pole, Q and use it to show that to locate the poles in the right half of s plane,  $\frac{R_2}{R_1}$  must be selected to be greater than 2.



1.0.2. Compare the basic structure for a sinusoidal oscillator with Wein-bridge oscillator and give expressions for A and  $\beta$ .

#### **Solution:**

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

• Comparring Fig 1.0.1 and Fig 1.0.2, we get

$$A = 1 + \frac{R_2}{R_1} \tag{1.0.2.1}$$

$$\beta = \frac{Z_p}{Z_p + Z_s} \tag{1.0.2.2}$$

where.

$$Z_p = \frac{R}{RSC + 1} \tag{1.0.2.3}$$

$$Z_s = \frac{RSC + 1}{SC}$$
 (1.0.2.4)

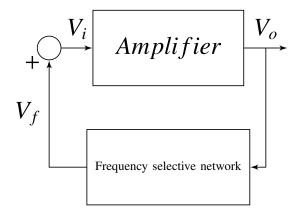


Fig. 1.0.2

1.0.3. Give the expression for loop gain for Weinbridge oscillator.

# **Solution:**

$$L(s) = A(s)\beta(s)$$
 (1.0.3.1)

$$L(s) = \frac{1 + \frac{R_2}{R_1}}{1 + Z_s Y_n} \tag{1.0.3.2}$$

$$L(s) = \frac{1 + \frac{R_2}{R_1}}{1 + (\frac{sRC + 1}{sC})(\frac{sRC + 1}{R})}$$
(1.0.3.3)

$$L(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{s^2 R^2 C^2 + sRC + sRC + 1}{sRC}}$$

$$L(s) = \frac{1 + \frac{R_2}{R_1}}{3 + sCR + \frac{1}{sCR}}$$
(1.0.3.4)

$$L(s) = \frac{1 + \frac{R_2}{R_1}}{3 + sCR + \frac{1}{sCR}}$$
 (1.0.3.5)

1.0.4. Write the characteristic equation for Wein-

bridge oscillator.

# **Solution:**

$$1 - L(s) = 0 \qquad (1.0.4.1)$$

$$1 - \frac{1 + \frac{R_2}{R_1}}{3 + sCR + \frac{1}{sCR}} = 0 \qquad (1.0.4.2)$$

$$3 + sRC + \frac{1}{sCR} = 1 + \frac{R_2}{R_1}$$
 (1.0.4.3)

$$3 - 1 + sRC + \frac{1}{sRC} - \frac{R_2}{R_1} = 0 \qquad (1.0.4.4)$$

$$2s + s^2RC + \frac{1}{RC} - s\frac{R_2}{R_1} = 0 (1.0.4.5)$$

$$s^2RC + s(2 - \frac{R_2}{R_1}) + \frac{1}{RC} = 0 (1.0.4.6)$$

$$s^2 + s \frac{1}{RC} (2 - \frac{R_2}{R_1}) + \frac{1}{R^2 C^2} = 0$$
 (1.0.4.7)

1.0.5. Write the general expression for the characteristic equation.

#### **Solution:**

$$s^2 + s\frac{\omega_0}{O} + \omega_0^2 = 0 ag{1.0.5.1}$$

1.0.6. State the **Barkhausen criterion** for sustained oscillations with frequency  $\omega_0$ .

# **Solution:**

$$L(j\omega_0) = A(j\omega_0)\beta(j\omega_0) = 1 \qquad (1.0.6.1)$$

- That is, at  $\omega_0$  the phase of the loop gain should be zero and the magnitude of loop gain should be 1.
- Only for a ∞ gain, system will produce a finite output for zero input.
- 1.0.7. Give the definition of **Quality factor**(Q) and explain its significance.

### **Solution:**

- It is a parameter of an oscillatory system expressing the relationship between stored energy and energy dissipation.
- The "purity" of output sine waves will be a function of the selectivity feedback network.
- That is, higher the value of Q for frequency selective network, the less the harmonic content of sine wave produced.
- 1.0.8. Compare the equations 1.0.4.7 and 1.0.5.1 and give expressions for Q and  $\omega_0$

# **Solution:**

$$\omega_0^2 = \frac{1}{R^2 C^2} \tag{1.0.8.1}$$

$$\omega_0 = \frac{1}{RC} \frac{\omega_0}{Q} = \frac{1}{RC} (2 - \frac{R_2}{R_1})$$
 (1.0.8.2)

$$Q = \frac{1}{(2 - \frac{R_2}{P_c})} \tag{1.0.8.3}$$

(1.0.8.4)

(1.0.4.4) 1.0.9. Using Eq 1.0.8.3 calculate the value of  $\frac{R_2}{R_1}$  for which poles lie on right hand of s-plane.

#### **Solution:**

Poles lie on imaginary axis for  $Q = \infty$ 

$$2 - \frac{R_2}{R_1} = 0 \tag{1.0.9.1}$$

$$\frac{R_2}{R_1} = 2 \tag{1.0.9.2}$$

... For poles to lie on right hand side of s-plane

$$\frac{R_2}{R_1} > 2 \tag{1.0.9.3}$$

1.0.10. Verify the above calculations using a Python code.

#### **Solution:**

codes/ee18btech11044 3 1.py

- This figure shows how the location of poles vary if  $\frac{R_2}{R_1}$  is varied for a fixed  $\omega_0$ .
- I have varied  $\frac{R_2}{R_1}$  from -10 to 10.

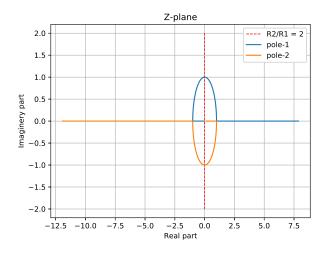


Fig. 1.0.10