

Control Systems

G V V Sharma*

CONTENTS

1 Feedback Circuits 1

Abstract—The objective of this manual is to introduce control system design at an elementary level.

1 FEEDBACK CIRCUITS

1.0.1. For the Wein-bridge oscillator of Fig 1.0.1, use the expression for loop gain in Eq 1.0.3.5 to find the poles of the closed-loop system. Give the expression for the pole, Q and use it to show that to locate the poles in the right half of s plane, $\frac{R_2}{R_1}$ must be selected to be greater than 2.

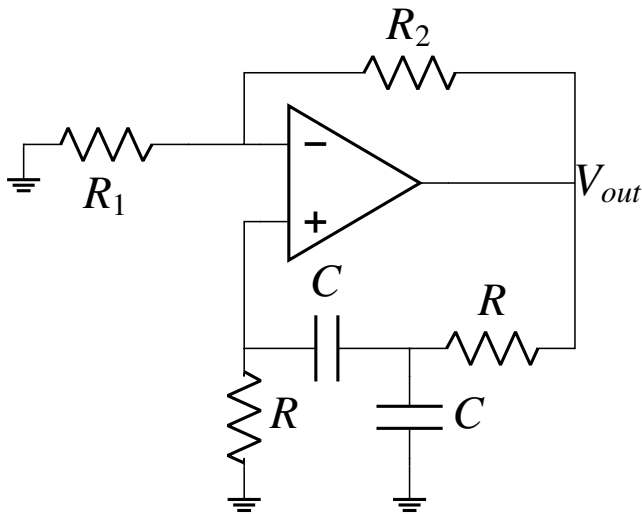


Fig. 1.0.1

1.0.2. Compare the basic structure for a sinusoidal oscillator with Wein-bridge oscillator and give expressions for G and H .

Solution:

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

• Comparing Fig 1.0.1 and Fig 1.0.2, we get

$$G = 1 + \frac{R_2}{R_1} \quad (1.0.2.1)$$

$$H = \frac{Z_p}{Z_p + Z_s} \quad (1.0.2.2)$$

where,

$$Z_p = \frac{R}{RSC + 1} \quad (1.0.2.3)$$

$$Z_s = \frac{RSC + 1}{SC} \quad (1.0.2.4)$$

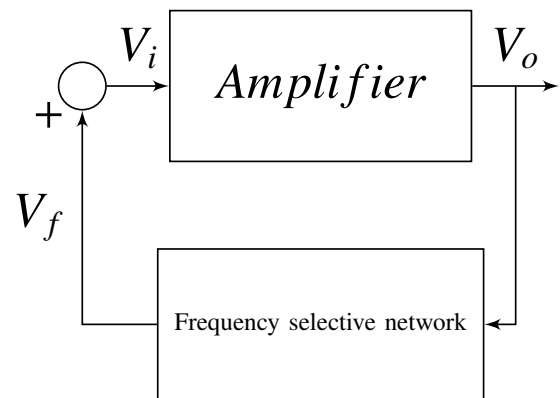


Fig. 1.0.2

1.0.3. Give the expression for loop gain for Wein-bridge oscillator.

Solution:

$$T(s) = A(s)\beta(s) \quad (1.0.3.1)$$

$$T(s) = \frac{1 + \frac{R_2}{R_1}}{1 + Z_s Y_p} \quad (1.0.3.2)$$

$$T(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \left(\frac{sRC+1}{sC}\right)\left(\frac{sRC+1}{R}\right)} \quad (1.0.3.3)$$

$$T(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{s^2 R^2 C^2 + sRC + sRC + 1}{sRC}} \quad (1.0.3.4)$$

$$T(s) = \frac{1 + \frac{R_2}{R_1}}{3 + sCR + \frac{1}{sCR}} \quad (1.0.3.5)$$

1.0.4. Write the characteristic equation for Wein-

bridge oscillator.

Solution:

$$1 - T(s) = 0 \quad (1.0.4.1)$$

$$1 - \frac{1 + \frac{R_2}{R_1}}{3 + sCR + \frac{1}{sCR}} = 0 \quad (1.0.4.2)$$

$$3 + sRC + \frac{1}{sCR} = 1 + \frac{R_2}{R_1} \quad (1.0.4.3)$$

$$3 - 1 + sRC + \frac{1}{sRC} - \frac{R_2}{R_1} = 0 \quad (1.0.4.4)$$

$$2s + s^2RC + \frac{1}{RC} - s\frac{R_2}{R_1} = 0 \quad (1.0.4.5)$$

$$s^2RC + s(2 - \frac{R_2}{R_1}) + \frac{1}{RC} = 0 \quad (1.0.4.6)$$

$$s^2 + s\frac{1}{RC}(2 - \frac{R_2}{R_1}) + \frac{1}{R^2C^2} = 0 \quad (1.0.4.7)$$

1.0.5. Write the general expression for the characteristic equation.

Solution:

$$s^2 + s\frac{\omega_0}{Q} + \omega_0^2 = 0 \quad (1.0.5.1)$$

1.0.6. State the **Barkhausen criterion** for sustained oscillations with frequency ω_0 .

Solution:

$$T(j\omega_0) = G(j\omega_0)H(j\omega_0) = 1 \quad (1.0.6.1)$$

- That is, at ω_0 the phase of the loop gain should be zero and the magnitude of loop gain should be 1.
- Only for a ∞ gain, system will produce a finite output for zero input.

1.0.7. Give the definition of **Quality factor(Q)** and explain its significance.

Solution:

- It is a parameter of an oscillatory system expressing the relationship between stored energy and energy dissipation.
- The "purity" of output sine waves will be a function of the selectivity feedback network.
- That is, higher the value of Q for frequency selective network, the less the harmonic content of sine wave produced.

1.0.8. Compare the equations 1.0.4.7 and 1.0.5.1 and give expressions for Q and ω_0

Solution:

$$\omega_0^2 = \frac{1}{R^2C^2} \quad (1.0.8.1)$$

$$\omega_0 = \frac{1}{RC} \quad (1.0.8.2)$$

$$\frac{\omega_0}{Q} = \frac{1}{RC}(2 - \frac{R_2}{R_1}) \quad (1.0.8.3)$$

$$Q = \frac{1}{(2 - \frac{R_2}{R_1})} \quad (1.0.8.4)$$

$$(1.0.8.5)$$

1.0.9. Using Eq 1.0.8.4 calculate the value of $\frac{R_2}{R_1}$ for which poles lie on right hand of s-plane.

Solution:

Poles lie on imaginary axis for $Q = \infty$

$$2 - \frac{R_2}{R_1} = 0 \quad (1.0.9.1)$$

$$\frac{R_2}{R_1} = 2 \quad (1.0.9.2)$$

\therefore For poles to lie on right hand side of s-plane

$$\frac{R_2}{R_1} > 2 \quad (1.0.9.3)$$

1.0.10. Verify the above calculations using a Python code.

Solution:

codes/ee18btech11044_3_1.py

- This figure shows how the location of poles vary if $\frac{R_2}{R_1}$ is varied for a fixed ω_0 .
- I have varied $\frac{R_2}{R_1}$ from -10 to 10.

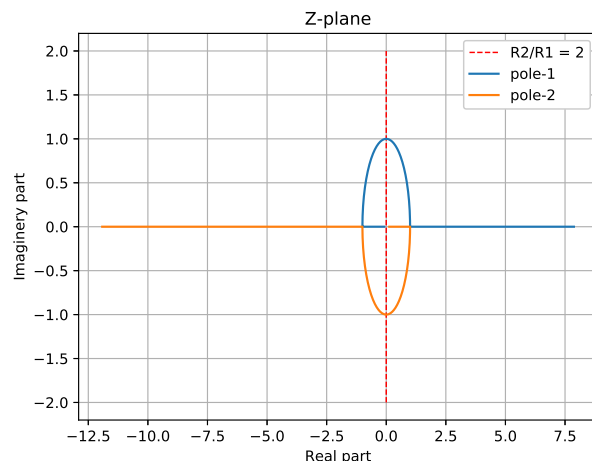


Fig. 1.0.10

1.0.11. Simulate the circuit shown in Fig 1.0.1 using spice simulators. Plot the output generated using python.

Solution:

You can find the netlist for the simulated circuit here:

spice/ee18btech11044.net

You can find the python script used to generate the output here:

codes/ee18btech11044_spice.py

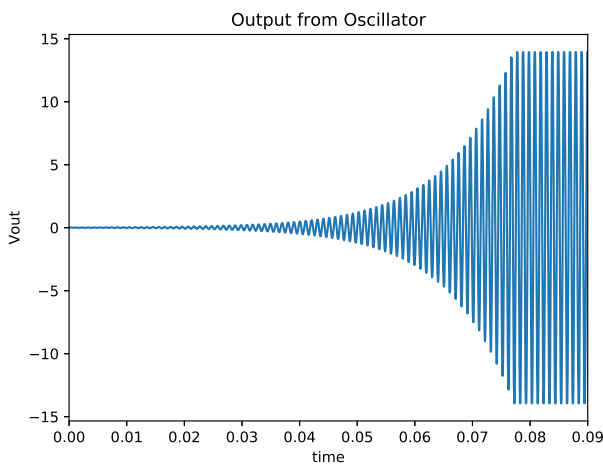


Fig. 1.0.11

1.0.12. Tabulate the values of Resistors and Capacitors you have chosen for the simulation.

Solution:

Parameter	Value
R_1	$10k\Omega$
R_2	$20.3k\Omega$
R_p	$10k\Omega$
R_s	$10k\Omega$
C_s	$16nF$
R_p	$10k\Omega$
C_p	$16nF$

TABLE 1.0.12

Where, according to Fig 1.0.1

$$R_p = R_s = R \quad (1.0.12.1)$$

$$C_p = C_s = C \quad (1.0.12.2)$$

1.0.13. Calculate the frequency of sinusoidal generated for the combination of R and C chosen using Eq 1.0.8.2

Solution:

Frequency generated is given by

$$\omega_0 = \frac{1}{RC} \quad (1.0.13.1)$$

$$\omega_0 = 6250 \text{ rad/sec} \quad (1.0.13.2)$$

$$f_0 = 995.22 \text{ Hz.} \quad (1.0.13.3)$$

1.0.14. Calculate the frequency of sinusoidal wave using plot generated from simulation.

Solution:

- Consider a part of plot generated from simulation shown in the Fig 1.0.14.
- Calculating the Time-period of the sinusoidal wave generated using the two points marked in the Fig 1.0.14.

$$T_0 = 0.0856452 - 0.0846361 \quad (1.0.14.1)$$

$$f_0 = 1/T_0 \quad (1.0.14.2)$$

$$f_0 = 990.98 \text{ Hz.} \quad (1.0.14.3)$$

- We get the frequencies calculated from the formulae and the plot to be approximately same.

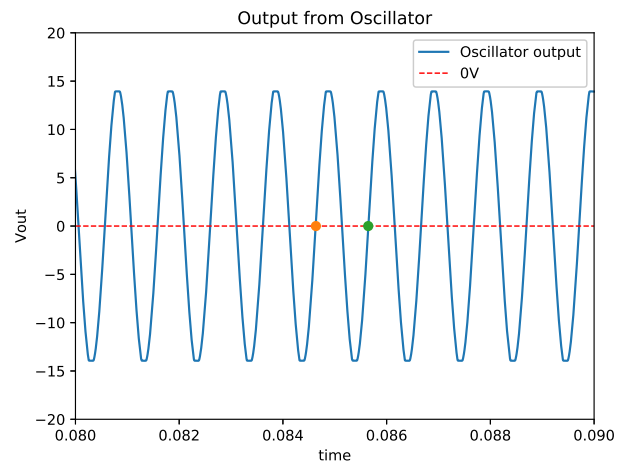


Fig. 1.0.14